
 


 THERE'S NO END IN SIGHT... NOW WE HAVE MICROS WITH THE POWER OF MINIS, "SUPERMINIS" THAT RIVAL MAINFRAMES, MINIS ON A CHIP... AND THERE'S TALK OF REDUCING COMPONENTS TO MOLECULAR SIZE USING RECOMBINANT DNA TECHNOLOGY...



THERE SEEMS TO BE NO SUCH THING AS A COMPUTER WITH TOO MUCH COMPUTING POWER. NO MATTER THE SPEED OR CAPACITY, COMPUTERS ALWAYS FIND JOBS TO DO... AND NO WONDER: THIS IS THE AGE OF EXCESS INFORMATION!



## PART II

# LOGICAL SPAGHETTI



COMPUTERS ARE LIKE ELEPHANTS: THERE ARE A LOT OF WAYS TO DESCRIBE THEM...


A POWERFUL CALCULATOR!

MADE OF SWITCHES!

IT FOLLOWS INSTRUCTIONS!

AN INPUT-OUTPUT DEVICE!


EXOTIC HARDWARE!

 

.....  
HOW DOES ONE GET TO THE HEART OF THE MATTER?

WITH AN ELEPHANT CLEAVER?



 


IF THERE'S ONE  
IDEA WE'VE TRIED  
TO DRUM IN,  
IT'S THAT THE  
COMPUTER IS  
ESSENTIALLY AN  
**INFORMATION  
PROCESSOR.**  
SO FORGET THE  
ELEPHANT...

TO UNDERSTAND INFORMATION PROCESSING, IT HELPS TO  
COMPARE IT WITH A MORE FAMILIAR PROCESS: **COOKING.**  
SO STEP INTO GRANDMOTHER BABBAGE'S KITCHEN, AS SHE  
PREPARES BASIC SPAGHETTI...



HERE'S THE WORLD FAMOUS RECIPE:

 **1** BRING A KETTLE  
OF SALTED WATER  
TO BOIL.




**2** ADD 8 OZ. OF RAW  
SPAGHETTI.



**3** BOIL FOR 10 MINUTES.



**4** DRAIN THROUGH A  
SIEVE.

 

**5** SERVE..



THIS SPAGHETTI  
IS BETTER ANALYZED  
THAN EATEN!

IT'S NOT HARD TO DISTINGUISH A FEW COMPONENTS IN THIS PROCESS:

FIRST, THE INGREDIENTS, OR **INPUT.**




NEXT, THE EQUIPMENT WHICH DOES THE COOKING: HANDS, KETTLE, STOVE, SALTSHAKER, SIEVE, PLATE, SPOON.




THESE FORM THE **PROCESSING UNIT.**

 LESS OBVIOUSLY, THERE IS A PART OF THE COOK'S BRAIN WHICH CONTROLS THE PROCESS. IT MONITORS AND DIRECTS THE STEP-BY-STEP UNFOLDING OF THE RECIPE. THIS IS REFERRED TO AS THE



 
**CONTROL UNIT.**

AND OF COURSE THE COMPLETED DISH, OR **OUTPUT.**




WHICH ALSO RESEMBLES THE COOK'S BRAIN...

 OF COURSE, SPAGHETTI IS NOTHING SPECIAL! ANY RECIPE COULD BE PROCESSED BY THE SAME BASIC STRUCTURE:




OR, MORE ABSTRACTLY:

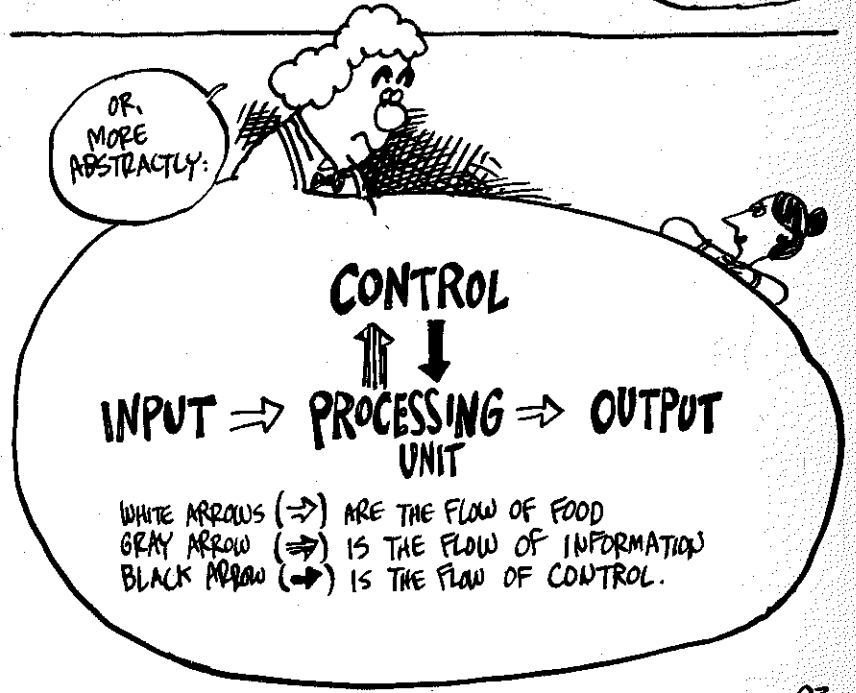


WITH COMPUTERS, THE DIAGRAM IS SLIGHTLY DIFFERENT:

 THERE ARE TWO REASONS FOR THIS: ONE IS THE FACT THAT INPUT AND OUTPUT ARE INFORMATION, NOT FOOD — SO THE GRAY ARROW IS THE SAME AS THE WHITE ONES.



 THE OTHER IS THE GREAT IMPORTANCE OF **MEMORY**, WHICH FORMS THE FIFTH AND FINAL COMPONENT. IN COMPUTERS, ALL INFORMATION PASSES INTO MEMORY FIRST! HERE'S THE DIAGRAM:




⇒ = INFORMATION FLOW

→ = CONTROL FLOW




IN THE CASE OF COMPUTERS, THE **INPUT** CONSISTS OF ALL THE "RAW" DATA TO BE PROCESSED — AS WELL AS THE ENTIRE "RECIPE," OR PROGRAM, WHICH SPECIFIES WHAT'S TO BE DONE WITH THEM.

 
THE **MEMORY** STORES THE INPUT AND RESULTS FROM THE PROCESSING UNIT:



 
**CONTROL** READS THE PROGRAM AND TRANSLATES IT INTO A SEQUENCE OF MACHINE OPERATIONS.



 THE **PROCESSING UNIT** PERFORMS THE ACTUAL ADDITIONS, MULTIPLICATION, COUNTING, COMPARISON, ETC, ON INFORMATION RECEIVED FROM MEMORY.




 THE **OUTPUT** CONSISTS OF THE PROCESSING UNIT'S RESULTS, STORED IN MEMORY AND TRANSMITTED TO AN OUTPUT DEVICE.



HERE'S THE REAL THING (AN IBM PERSONAL COMPUTER), JUST TO GIVE ONE EXAMPLE OF HOW THESE COMPONENTS MAY ACTUALLY LOOK:

 CONTROL, PROCESSING UNIT, AND MEMORY ARE HOUSED IN ONE SMALL BOX.



INPUT IS ENTERED FROM KEYBOARD.

DISK DRIVES PROVIDE EXTRA MEMORY STORAGE

OTHER COMMON INPUT/OUTPUT DEVICES (NOT PICTURED) ARE A **MODEM**, FOR SENDING AND RECEIVING SIGNALS OVER THE PHONE, AND A **PRINTER**, FOR PRODUCING OUTPUT ON PAPER.

LET'S START IN THE MIDDLE, WITH THE

# PROCESSING UNIT:

IN THE KITCHEN, A CHEF MAY DISPLAY A RICH REPERTOIRE OF PROCESSING POSSIBILITIES:

BRASE  
BROIL  
SAUTE  
ROAST  
POACH  
STEAM  
BOIL  
FRY  
BAKE...




BUT, AS THE GREAT ESCOFFIER HIMSELF HAS REMARKED, ALL COOKING TECHNIQUES ARE COMBINATIONS OF SIMPLER STEPS: THE APPLICATION OF MORE OR LESS HEAT, WET OR DRY, ETC...

THESE FEW ARE ELEMENTARY!



 LIKewise, ALL THE POWER OF THE COMPUTER DEPENDS ON A COUPLE OF ELEMENTARY OPERATIONS.




O.K... O.K... NO MORE BEATING AROUND THE BUSH WITH CULINARY METAPHORS...

THE COMPUTER'S ELEMENTARY OPERATIONS ARE

 **LOGICAL**



WHAT'S A LOGICAL OPERATION, YOU ASK? A LOGICAL QUESTION, CONSIDERING HOW MUCH EASIER IT IS TO THINK OF ILLOGICAL OPERATIONS, LIKE AMPUTATION OF THE THUMBS OR GETTING OUT OF BED ON MONDAYS...



TO EVERYONE'S GOOD FORTUNE, LOGIC ISN'T AS HARD AS IT USED TO BE. IN ARISTOTLE'S TIME, THE SUBJECT WAS DIVIDED INTO INDUCTIVE AND DEDUCTIVE BRANCHES, INDUCTIVE LOGIC BEING THE ART OF INFERRING TRUTHS BY OBSERVING NATURE, WHILE DEDUCTIVE LOGIC DEDUCED TRUTHS FROM OTHER TRUTHS:

1. YOU ARE A MAN.
2. ALL MEN ARE MORTAL.
3. THEREFORE, YOU ARE MORTAL.

∴ AHEM ∴  
HOW DO YOU KNOW ALL MEN ARE MORTAL??



### MEDIEVAL

LOGICIANS COMPOUNDED THE CONFUSION WITH SIX "MODES": A STATEMENT WAS EITHER TRUE, FALSE, NECESSARY, CONTINGENT, POSSIBLE, OR IMPOSSIBLE.



NECESSARY IS TO CONTINGENT AS TRUE IS TO FALSE... POSSIBLY...

THEIR REASONING GREW SO MINDLESS THAT THE MEDIEVAL LOGICIAN DUNS SCOTUS HAS BEEN IMMORTALIZED IN THE WORD "DUNCE"!

THE SUBJECT WAS STRETCHED  
TO ABSURD LENGTHS  
BY LEWIS  
CARROLL:

- (1) GENTILES  
HAVE NO  
OBJECTION  
TO PORK.
- (2) NOBODY WHO  
ADMIRES PIGSTIES  
EVER READS  
HOGG'S POEMS.
- (3) NO  
MANDARIN  
KNOWS HEBREW.
- (4) EVERYONE, WHO  
DOES NOT OBJECT  
TO PORK, ADMIRE  
TURNSTILES.
- (5) NO JEW IS  
IGNORANT  
OF HEBREW.

THEREFORE, NO  
MANDARIN EVER  
READS HOGG'S  
POEMS. " \*

CLEARLY, IT WAS  
TIME TO SIMPLIFY  
THE SUBJECT...

\* FROM SYMBOLIC LOGIC

THIS STEP WAS  
TAKEN BY

GEORGE  
BOOLE (1815-  
1864),

AN ENGLISH MATHEMATICIAN  
WHO BUILT AN  
"ALGEBRA" OUT OF  
LOGIC.



THAT IS, HE MADE  
LOGIC FULLY  
SYMBOLIC, JUST  
LIKE MATH. SENTENCES  
WERE DENOTED BY LETTERS  
AND CONNECTED BY  
ALGEBRAIC SYMBOLS — AN  
IDEA GOING BACK TO  
LEIBNIZ, WHO HAD DREAMED  
OF "JUSTICE BY ALGEBRA."



$$(1-x)(1-y) = 1-x-y+xy.$$

THEREFORE, 30 YEARS!


WE CAN'T POSSIBLY DESCRIBE BOOLE'S ALGEBRA IN ITS  
ENTIRETY. WE'LL LIMIT OURSELVES TO THREE WORDS:

AND,  
OR,  
NOT!



 BOOLE LOOKED AT  
THE VERY  
CONNECTIVE TISSUE  
OF LANGUAGE:  
THE WORDS "AND",  
"OR", AND "NOT".





SUPPOSE P IS ANY STATEMENT... FOR EXAMPLE,

P = "The pig has spots."

ACCORDING TO BOOLE, THIS SENTENCE IS EITHER TRUE (T) OR FALSE (F). NO OTHER OPTION IS ALLOWED! \*



NOW LET Q BE ANOTHER STATEMENT—LIKELIKE TRUE OR FALSE:

Q = "The pig is glad."



NOW FORM THE COMPOUND SENTENCES:

P AND Q = THE PIG IS SPOTTED AND THE PIG IS GLAD.

P OR Q = THE PIG IS SPOTTED OR THE PIG IS GLAD.

WHEN ARE THESE SENTENCES TRUE?



\* IN SOME VERSIONS OF LOGIC, MORE THAN TWO TRUTH VALUES ARE PERMISSIBLE.


THERE ARE FOUR POSSIBLE COMBINATIONS OF TRUTH AND FALSEHOOD FOR P AND Q:



P TRUE, Q TRUE



P FALSE, Q TRUE

 

P TRUE, Q FALSE



P FALSE, Q FALSE

**AND**

"THE PIG IS GLAD AND HAS SPOTS."

THIS IS TRUE ONLY IN THE ONE CASE IN WHICH P, Q ARE BOTH TRUE. THIS IS SUMMARIZED IN A TRUTH TABLE:



P	Q	P AND Q
T	T	T
T	F	F
F	T	F
F	F	F

**OR**

"THE PIG IS GLAD OR HAS SPOTS."

THIS IS TRUE IN THE THREE CASES FOR WHICH EITHER ONE OF THE STATEMENTS P, Q IS TRUE.



P	Q	P OR Q
T	T	T
T	F	T
F	T	T
F	F	F

AND ONE MORE LOGICAL OPERATOR—

# NOT

NOT-P = The pig is NOT spotted.

THIS OPERATOR  
SIMPLY  
TURNS A  
STATEMENT  
INTO ITS  
OPPOSITE.



P	NOT-P
T	F
F	T

BOOLE MADE THIS LOOK ALGEBRAIC IN SOMETHING LIKE THE FOLLOWING WAY:

- ★ DENOTE T BY 1
- ★ DENOTE F BY 0
- ★ DENOTE AND BY  $\cdot$
- ★ DENOTE OR BY  $\oplus$
- ★ DENOTE NOT BY  $\bar{\phantom{x}}$

THEN THE TRUTH TABLES BECOME:

$1 \cdot 1 = 1$	$1 \oplus 1 = 1$	$1 - 1 = 0$
$1 \cdot 0 = 0$	$1 \oplus 0 = 1$	$1 - 0 = 1$
$0 \cdot 1 = 0$	$0 \oplus 1 = 1$	
$0 \cdot 0 = 0$	$0 \oplus 0 = 0$	





EXCEPT FOR THE ONE WEIRD EQUATION  $1 \oplus 1 = 1$ , THESE LOOK LIKE ORDINARY ARITHMETIC... WITH "AND" PLAYING THE ROLE OF "TIMES" AND "OR" IN THE ROLE OF "PLUS."



WE'RE NEVER GOING TO USE THE SYMBOLS  $\cdot$  AND  $\oplus$ ... YOU CAN FORGET ABOUT THEM... BUT USING 1 AND 0 TO REPRESENT TRUE AND FALSE IS VERY USEFUL... SO FROM NOW ON WE'LL WRITE TRUTH TABLES LIKE THIS:


P	Q	P AND Q	P OR Q	P	NOT-P
1	1	1	1	1	0
1	0	0	1	0	1
0	1	0	1		
0	0	0	0		

  FROM THESE RELATIONSHIPS, BOOLE BUILT UP AN ENTIRE ALGEBRA, USING ONLY THE NUMBERS 0 AND 1... TODAY THIS **BOOLEAN ALGEBRA** IS USED ALL THE TIME BY COMPUTER ENGINEERS — ONLY THEY EXPRESS IT AS ELECTRICAL CIRCUITS.




THE KEY IS THE **AUTOMATIC SWITCH**, WHICH IS EITHER OPEN OR CLOSED, AS A LOGICAL PROPOSITION IS EITHER TRUE OR FALSE.

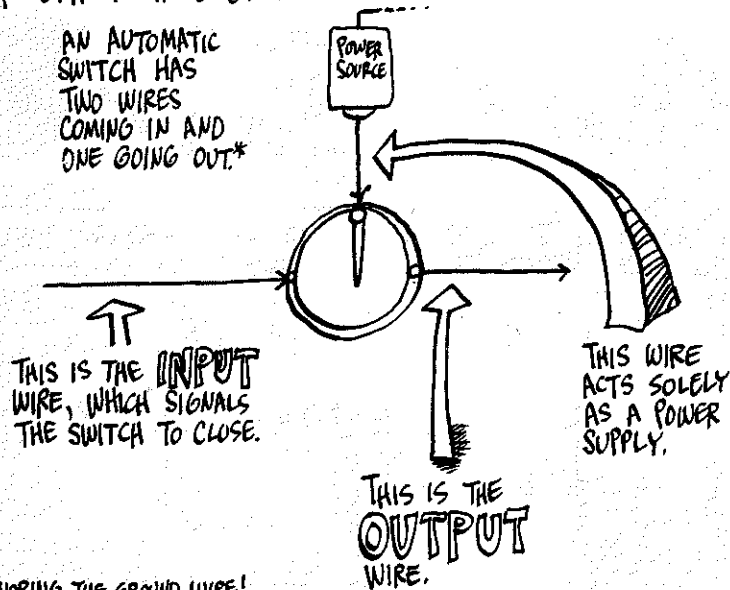AN AUTOMATIC SWITCH HAS TWO WIRES COMING IN AND ONE GOING OUT.\*




\*IGNORING THE GROUND WIRE!

 WHEN NO CURRENT FLOWS THROUGH THE INPUT WIRE, THE SWITCH REMAINS OPEN, AS PICTURED ABOVE. WHEN AN INPUT SIGNAL ARRIVES, HOWEVER, THE ELECTRONIC EQUIVALENT OF A MINIATURE BOXING GLOVE "PUNCHES" THE SWITCH CLOSED, RESULTING IN AN OUTPUT SIGNAL.



 WHAT IS THE OUTPUT WHEN TWO SWITCHES (A, B) ARE ARRANGED IN SERIES, ONE AFTER THE OTHER? [IN OUR DIAGRAM, PLEASE NOTE THE REARRANGEMENT OF WIRES, MADE FOR CONVENIENCE OF ILLUSTRATION.]



THE CURRENT CAN FLOW ONLY IF **BOTH** SWITCHES ARE CLOSED — I.E., WHEN INPUT SIGNALS ARRIVE SIMULTANEOUSLY AT A AND B.


WRITING 1 FOR CURRENT AND 0 FOR NO CURRENT, WE CAN THEN WRITE THIS **INPUT-OUTPUT** TABLE. LOOK FAMILIAR? IT SHOULD! IT'S IDENTICAL TO THE TRUTH TABLE FOR **AND!**

A	B	OUTPUT
1	1	1
1	0	0
0	1	0
0	0	0


THAT'S WHY THIS ARRANGEMENT OF SWITCHES IS CALLED AN

**AND-GATE**

AND IT HAS ITS VERY OWN SYMBOL

 

 TWO SWITCHES CONNECTED IN PARALLEL BEHAVE LIKE LOGICAL **OR**: CURRENT CAN PASS FROM POWER TO OUTPUT IF EITHER SWITCH A, B IS CLOSED (OR IF BOTH ARE).




A	B	OUTPUT
1	1	1
1	0	1
0	1	1
0	0	0


THIS IS THE

**OR-GATE**

AND ITS SYMBOL IS:

 


 **NOT** IS NOT ANY MORE DIFFICULT... IT USES A SPECIAL SWITCH THAT REMAINS CLOSED UNTIL AN INPUT SIGNAL OPENS IT — JUST THE REVERSE OF AN ORDINARY SWITCH:



A	OUTPUT
1	0
0	1

 THIS KIND OF SWITCH IS CALLED AN **INVERTER**, AND IT HAS A SYMBOL, TOO:




AN EVERYDAY EXAMPLE SHOWS HOW THESE SIMPLE GATES CAN MAKE LOGICAL DECISIONS.

YOU KNOW THOSE BUZZERS THAT GO OFF WHEN YOU START YOUR CAR AND YOUR SEAT BELT ISN'T FASTENED? THE KIND THAT'S SPECIALLY DESIGNED TO PENETRATE HUMAN BONE?



 WELL, THAT'S BECAUSE THE SEAT BELT AND IGNITION ARE CONNECTED BY AN **AND-GATE**, LIKE SO:



THAT IS, **IF** THE IGNITION IS ON **AND** THE SEAT BELT IS **NOT**, THE BUZZER SOUNDS! PRETTY LOGICAL, NO?

CAN YOU THINK OF ANY EXAMPLES OF OR-GATES IN DAILY LIFE?

NOT AT THE MOMENT... I'M BUSY!




(HOW ABOUT A SMOKE ALARM TRIGGERED BY EITHER OF TWO DIFFERENT DETECTORS?)




HERE ARE A FEW WARM-UP EXERCISES FOR CHASING THROUGH LOGIC DIAGRAM:


DO THE INPUT-OUTPUT (I/O) TABLES:

 

(7) WHAT IS OUTPUT WHEN A=1, B=0, C=1?

 

(8) COMPLETE THE I/O TABLE:

 

A	B	C	D	E	F
1	1	1	0	0	0
1	0	0	1	0	0
0	1	0	0	1	0
0	0	0	0	0	1

DESIGN LOGIC DIAGRAMS WITH THESE I/O TABLES.

(9) 

IN	OUT
1 0	0
0 0	0
0 0	0

 (10) 

IN	OUT
1 1	0
1 0	1
0 0	1
0 0	1


 (11) 

IN	OUT
1 0	1
0 0	1
0 0	1
0 0	1

 (12) 

IN	OUT
1 0	0
0 0	0
0 0	0
0 0	0

 LOGIC GATES HAVE ONLY ONE OR TWO INPUTS AND A SINGLE OUTPUT — BUT COMPUTER COMPONENTS HAVE MANY INPUTS AND OUTPUTS WITH COMPLICATED INPUT/OUTPUT BEHAVIOR:



THE WONDERFUL FACT IS THAT ANY INPUT/OUTPUT TABLE CAN BE PRODUCED BY A COMBINATION OF LOGIC GATES!


TO DO IT, YOU NEED MULTIPLE-INPUT LOGIC GATES. HERE'S A 4-INPUT AND-GATE:



A	B	C	D	E
1	1	1	1	1
1	1	1	0	0
1	1	0	1	0
1	0	1	1	0
0	0	0	0	0

ALL 0's

 THIS MEANS E=1 IF A=B=C=D=1, AND E=0 OTHERWISE. THE GATE CAN BE MADE WITH FOUR SWITCHES IN SERIES:




SIMILARLY, THERE'S A MULTIPLE-INPUT OR-GATE:



A	B	C	D	E
1	1	1	1	1
1	1	1	0	1
1	1	0	1	1
1	0	1	1	1
0	0	0	1	1
0	0	0	0	0

ALL 1's

 IT CAN ACTUALLY BE MADE FROM AN AND-GATE AND SOME INVERTERS:



AS AN EXAMPLE OF HOW TO PRODUCE A GIVEN INPUT/OUTPUT TABLE, LET'S SOLVE PROBLEM #12:

IN		OUT
A	B	C
1	1	0
1	0	1
0	1	1
0	0	0

BEGIN BY FINDING ALL ROWS WHERE  $C=1$ .

THE TABLE SAYS  $C=1$  IF  $A=1$  AND  $B=0$  OR  $A=0$  AND  $B=1$ .  
 $C=0$  OTHERWISE.


WRITING  $\bar{A}$  FOR NOT-A, THIS AMOUNTS TO SAYING

$C=1$  IF  $A=1$  AND  $\bar{B}=1$  OR  $\bar{A}=1$  AND  $B=1$ .  
 $C=0$  OTHERWISE.

IN OTHER WORDS,

$$C = (A \text{ AND } \bar{B}) \text{ OR } (\bar{A} \text{ AND } B)$$

 TO DRAW THE CIRCUIT, RUN THE INPUT WIRES AND THEIR NEGATIVES IN ONE DIRECTION —



—AND ATTACH THE GATES TO THE APPROPRIATE WIRES.

EXACTLY THE SAME METHOD WORKS FOR MORE INPUTS. FOR EXAMPLE:

A	B	C	D
1	1	1	0
1	0	1	0
0	1	1	0
0	0	0	1
0	0	0	1
0	0	0	1
0	0	0	1


AGAIN, FIND ALL ROWS WITH OUTPUT = 1.

NOTE ALL POSSIBLE INPUT COMBINATIONS!

IN THIS CASE,


$D = (A \text{ AND } B \text{ AND } C) \text{ OR } (A \text{ AND } \bar{B} \text{ AND } \bar{C}) \text{ OR } (\bar{A} \text{ AND } B \text{ AND } \bar{C}) \text{ OR } (\bar{A} \text{ AND } \bar{B} \text{ AND } C)$ .

 RUN THE INPUTS AND THEIR NEGATIVES ACROSS THE PAGE, ATTACH AND-GATES, THEN RUN THEM THROUGH AN OR-GATE!





TO REPEAT: BY THE SAME METHOD, YOU CAN PRODUCE INPUT/OUTPUT TABLE!!

WHERE DOES THIS LEAVE US?

 


  BY NOW YOU MAY BE GETTING THE IDEA THAT INFORMATION IS ENCODED INSIDE COMPUTERS AS STRINGS OF 1'S AND 0'S, WHICH CAN BE TRANSFORMED IN ANY WAY WE LIKE BY THE RIGHT COMBINATION OF LOGIC GATES.



BUT WE HAVEN'T REALLY SEEN HOW LOGIC GATES CAN DO THE JOB COMPUTERS WERE DESIGNED FOR:

NAMELY: HOW DO COMPUTERS COMPUTE?

 

The questions:

□ IS THERE SOME NATURAL WAY TO REPRESENT NUMBERS USING ONLY 0'S AND 1'S? CAN THE OPERATIONS OF ARITHMETIC BE BUILT OUT OF LOGIC?

The answer

(WHICH GOES BACK TO OUR OLD PAL LEIBNIZ):



AS SURE AS I DIDN'T STEAL CALCULUS FROM NEWTON!


THE SYSTEM IS CALLED

# BINARY NUMBERS.

THEY'RE BASED ON TWO!

OUR DECIMAL SYSTEM, BASED ON TEN, WAS A RESULT OF OUR HAVING TEN FINGERS — AN ACCIDENT OF NATURE! BINARY NUMBERS ARE WHAT WOULD HAVE EVOLVED IF WE'D BEEN BORN WITH TWO FINGERS, LIKE THE TREE SLOTH.

 I'D COUNT BY FOURS, BUT I ONLY HAVE ONE FREE PAW!



TREE SLOTS ALWAYS COUNT IN BINARY!

# 10


LOOK AT THE SYMBOL "10" - "ONE-ZERO." FORGET THAT IT USUALLY MEANS TEN! FORGET IT! STOP CALLING IT THAT! IS THERE ANYTHING THERE THAT SAYS "TEN?"

**NO!!** IT'S JUST A ONE FOLLOWED BY A ZERO - IN AND OF ITSELF, IT HAS NOTHING TO DO WITH TEN!!!

THE SYMBOL ONLY MAKES "TEN" FLASH THROUGH YOUR MIND BECAUSE YOU'VE ALWAYS CALLED IT THAT... IT'S LIKE A RITUAL: PERFORM IT OVER AND OVER AND IT BECOMES AUTOMATIC!



IN ACTUALITY, "10" MEANS:

 


| (ONE) HANDFUL\* AND  
 ○ (ZERO) FINGERS LEFT OVER

\*REMEMBER - ON P. 24, WE AGREED TO CALL TEN FINGERS, NOT FIVE, A HUMAN HANDFUL!



SINCE WE HUMANS HAVE TEN FINGERS, OUR "10" IS TEN... BUT TO AN ORGANISM WITH, SAY, EIGHT FINGERS, 10 WOULD MEAN EIGHT!

 IN THE CASE AT HAND, WITH JUST TWO FINGERS IN A HANDFUL... 10 MEANS **TWO!**



SO WE CAN WRITE:


$$10_{\text{BINARY}} = 2_{\text{DECIMAL}}$$



 NOTE: DO NOT READ THIS AS "TEN EQUALS TWO." TEN DOES NOT EQUAL TWO!! "ONE-ZERO IN BINARY" EQUALS TWO!!







LIKEWISE, 100 — "ONE-ZERO-ZERO" — MEANS

1 HANDFUL OF HANDFULS.

IN DECIMAL, THAT'S  $10 \times 10$ , OR A HUNDRED. WELL, IN BINARY IT'S  $10 \times 10$  ALSO — BUT THAT ONLY AMOUNTS TO **FOUR!**

1000 IS

$$10 \times 10 \times 10 = 2 \times 2 \times 2 = 8$$

AND GENERALLY,

1 FOLLOWED BY N ZEROS IS:

$$2 \times \dots \times 2 = 2^N$$

N TIMES

("TWO TO THE N<sup>TH</sup> POWER").

IN THE COMPUTER AGE, EVERYONE WILL BE REQUIRED BY LAW TO MEMORIZE THE POWERS OF TWO, UP TO  $2^{10}$ . BETTER NOT WAIT! AVOID JAIL AND DO IT NOW!

- $1 = 2^0 = 1$
- $10 = 2^1 = 2$
- $100 = 2^2 = 4$
- $1000 = 2^3 = 8$
- $10000 = 2^4 = 16$
- $100000 = 2^5 = 32$
- $1000000 = 2^6 = 64$
- $10000000 = 2^7 = 128$
- $100000000 = 2^8 = 256$
- $1000000000 = 2^9 = 512$
- $10000000000 = 2^{10} = 1024$



ALL OTHER BINARY NUMBERS — 101, 1111, 11000, AND EVERY OTHER PATTERN OF 0'S AND 1'S — IS A SUM OF SUCH POWERS OF TWO! IT'S COMPLETELY ANALOGOUS TO DECIMAL.

IN DECIMAL:

$$\begin{array}{r} 497 = \\ \hline 400 \\ + 90 \\ + 7 \end{array}$$

IN BINARY:

$$\begin{array}{r} 111110001 = \\ \hline 100000000 \\ + 100000000 \\ + 100000000 \\ + 100000000 \\ + 100000000 \\ + 10000 \\ + 1 \end{array} \left. \vphantom{\begin{array}{r} 111110001 \\ \hline 100000000 \\ + 100000000 \\ + 100000000 \\ + 100000000 \\ + 100000000 \\ + 10000 \\ + 1 \end{array}} \right\} \begin{array}{r} 256 \\ 128 \\ 64 \\ 32 \\ 16 \\ 1 \\ \hline 497 \end{array}$$

TO TRANSLATE A BINARY NUMBER INTO THE DECIMAL SYSTEM, LIST THE POWERS OF TWO OVER THE CORRESPONDING PLACES, AND ADD THOSE LYING OVER A 1.

$$\begin{array}{r} \dots 2^{10} \ 2^9 \ 2^8 \ 2^7 \ 2^6 \ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \\ \hline 1 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0 \\ 256 + 16 + 8 + 2 = 282 \end{array}$$

NOW YOU DO IT. CONVERT TO DECIMAL:

- (1) 11 (2) 101 (3) 111111 (4) 11010101011101




ANOTHER WONDERFUL FACT ABOUT BINARY:

 
**SUBTRACTION IS DONE BY ADDING !!**



THE METHOD IS CALLED USING "TWO'S COMPLEMENT." FIRST YOU INVERT THE NUMBER TO BE SUBTRACTED, SO THAT ALL ITS 1'S BECOME 0'S AND VICE VERSA. THEN ADD THE TWO NUMBERS AND ADD 1 TO THE SUM. IGNORE THE FINAL CARRY AND THAT'S THE ANSWER!




 BINARY MULTIPLICATION — AND ANY MULTIPLICATION — MAY ALSO BE DONE BY REPEATED ADDITION: TO MULTIPLY A × B, JUST ADD A TO ITSELF B TIMES. LIKEWISE, DIVISION CAN BE DONE BY REPEATED SUBTRACTION.




The computer can do all arithmetic by adding !!

# The ADDER

 

 BEFORE SHOWING HOW TO COMBINE LOGIC GATES INTO A BINARY ADDER, WE NEED A BIT OF TERMINOLOGY.



BIT? DID SOMEONE SAY "BIT?"

**BIT** IS AN ABBREVIATION OF "BINARY DIGIT." IT REFERS TO A SINGLE 0 OR 1.

IS IT BINARY DIGIT OR BINARY DIGIT?

IT'S VERY COMMON TO GROUP BITS EIGHT AT A TIME, AND ANY STRING OF EIGHT BITS IS CALLED A **BYTE**. THERE ARE 2<sup>8</sup> OR 256, POSSIBLE BYTES, FROM 00000000 TO 11111111.

NOW LET'S SEE  
WHAT AN ADDER  
MIGHT LOOK LIKE.

THIS ADDER LOOKS LIKE  
A POISONOUS ROSE...



TO SAVE DRAWING, WE'LL MAKE IT A FOUR-BIT ADDER, CAPABLE  
OF ADDING TWO 4-BIT NUMBERS,  
OR "NIBBLES." (YES, THEY'RE  
REALLY CALLED THAT!)



$$\begin{array}{r} A = 1110 \\ B = 1011 \\ \hline 11001 \end{array}$$

THE INPUT OF OUR ADDER MUST  
CONSIST OF EIGHT BITS, FOUR FOR EACH  
NIBBLE. THE OUTPUT MUST  
BE FIVE BITS, THAT IS, A NIBBLE  
PLUS ONE BIT FOR A POSSIBLE CARRY.  
LIKE SO:



ANY NUMBER  
FROM ZERO TO  
FIFTEEN

ANY NUMBER  
FROM ZERO TO  
THIRTY

HOW TO PROCEED? ONE WAY IS TO MAKE A GIANT TRUTH TABLE,  
MATCHING EVERY POSSIBLE COMBINATION OF INPUTS WITH THE  
CORRECT OUTPUT, AND CONSTRUCTING A HUGE STEW OF ANDs  
AND NOTs TO FORCE A SOLUTION. THIS IS  
POSSIBLE, BUT THE COMPLEXITY OF THE TASK MIGHT  
MAKE YOU THROW UP YOUR HANDS.

OR JUST  
THROW UP,  
IF YOU  
HAVE NO  
HANDS!


INSTEAD, RECALL HOW  
ADDITION WORKS  
IN PRACTICE:  
COLUMN BY  
COLUMN, WITH  
A CARRY  
BIT CARRYING  
OUT OF ONE  
COLUMN AND  
INTO THE NEXT:

1	1	1	0
1	0	1	1
1	1	0	0
1	1	0	0


SO IT  
SHOULD BE  
POSSIBLE TO  
MAKE A  
4-BIT ADDER  
OUT OF FOUR  
1-BIT ADDERS!



 THE 1-BIT  
ADDER MUST HAVE  
THREE INPUTS -  
ONE FOR EACH OF  
THE TWO SUMMAND  
BITS AND ONE FOR  
THE BIT CARRIED  
IN - AND TWO  
OUTPUTS - ONE  
SUM BIT AND  
ONE CARRY-OUT  
BIT.



 FOUR OF THESE CAN THEN BE HOOKED UP TO PRODUCE A  
4-BIT ADDER:



NOTE:  
8 INPUTS  
AND 5  
OUTPUTS, AS  
PROMISED!




AND WHAT ABOUT NON-NUMERICAL INFORMATION — THE ALPHABET, PUNCTUATION MARKS, OTHER SYMBOLS, AND EVEN THE BLANK SPACE ??

SINCE THERE IS NO NATURAL WAY TO ENCODE THESE INTO 0'S AND 1'S, COMPUTER SCIENTISTS INVENTED AND ADOPTED A STANDARD CODE BY MUTUAL AGREEMENT:
 
# ASCII,

THE AMERICAN STANDARD CODE FOR INFORMATION INTERCHANGE.

(ACTUALLY, ASCII IS USED BY EVERYONE BUT IBM, WHICH HAS ITS OWN CODE, CALLED EBCDIC.)



FIRST THREE BITS


	0	0	0	0	1	1	1	1
	0	0	1	1	0	0	1	1
	0	1	0	1	0	1	0	1
NEXT FOUR BITS	0000	NUL	DLE	SP	@	P	'	P
	0001	SOH	DC1	!	1	A	Q	a
	0010	STX	DC2	"	2	B	R	b
	0011	ETX	DC3	#	3	C	S	c
	0100	EOT	DC4	\$	4	D	T	d
	0101	ENQ	NAK	%	5	E	U	e
	0110	ACK	SYN	&	6	F	V	f
	0111	BEL	ETB	'	7	G	W	g
	1000	BS	CAN	(	8	H	X	h
	1001	HT	EM	)	9	I	Y	i
	1010	LF	SUB	*	:	J	Z	j
	1011	VT	ESC	+	;	K	[	k
	1100	FF	FS	,	<	L	\	l
	1101	CR	GS	-	=	M	]	m
	1110	SO	RS	.	>	N	^	n
	1111	SI	US	/	?	O	-	o
								DEL

★ THUS, THE LETTER "T" IS ENCODED AS 101 0100... ETC!  
 ★ THE FIRST TWO COLUMNS CONTAIN SYMBOLS FOR SUCH THINGS AS "START OF HEADING" (SOH) AND OTHER TEXTUAL DIRECTIONS.

TO ENCODE AND DECODE DATA, COMPUTERS USE LOGIC DEVICES CALLED, NATURALLY ENOUGH, ENCODERS AND DECODERS.

 
## AN ENCODER

USUALLY HAS MANY INPUTS AND A FEW OUTPUTS. A SINGLE INPUT SIGNAL PRODUCES A PATTERN OF OUTPUTS. FOR EXAMPLE, A COMPUTER KEYBOARD IS ATTACHED TO AN ENCODER WHICH TRANSLATES A SINGLE KEYSTROKE INTO ITS ASCII CODE.



 
## A DECODER

WORKS THE OTHER WAY AROUND, TRANSLATING A PATTERN OF BITS INTO A SINGLE OUTPUT SIGNAL. ONE DECODER CONVERTS A BINARY NIBBLE INTO A DECIMAL DIGIT. ANOTHER TRANSFORMS A SPECIFIED LOCATION, OR ADDRESS, IN MEMORY INTO A SIGNAL TO THAT MEMORY CELL. (SEE P. 155.)




ONCE ALPHANUMERIC INFORMATION IS ENCODED IN BINARY STRINGS, IT IS READY TO BE PROCESSED BY THE COMPUTER'S MOST ELABORATE COMBINATION OF LOGIC GATES, THE
 
# ARITHMETIC LOGIC UNIT UNIT (OR ALU, FOR SHORT)




THIS IS THE MACHINE'S CENTRAL PROCESSOR, WHICH CAN ADD, SUBTRACT, MULTIPLY, COMPARE, SHIFT, AND PERFORM A WEALTH OF OTHER LOGICAL FUNCTIONS. THE DRAWING ABOVE REPRESENTS AN 8-BIT ALU, BUT THEY CAN RANGE FROM FOUR TO SIXTY BIT CAPABILITY, DEPENDING ON THE COMPUTER.

 THE FUNCTION SELECT INPUTS DETERMINE WHICH ARITHMETIC OR LOGICAL FUNCTION THE ALU IS TO PERFORM, EACH FUNCTION HAVING ITS OWN BINARY CODE. FOR EXAMPLE, 0001 APPLIED TO FUNCTION SELECT MIGHT MEAN **ADD**, IN WHICH CASE



 ANOTHER FUNCTION (0101, SAY) MIGHT **COMPARE** TWO BYTES, BIT BY BIT, AND OUTPUT A 1 WHEREVER THEY AGREE. (MEANWHILE, THE ADDER TAKES A NAP.)




YOU CAN GET AN IDEA OF A FANCY ALU'S CAPABILITIES FROM THE LIST ON PAGE 182.



THE ALU WOULD BE A COMPLETE CENTRAL PROCESSING UNIT, EXCEPT FOR ONE THING: IT'S UNABLE TO STORE RESULTS. RETURNING TO THE COOKING ANALOGY, WE MIGHT SAY THE ALU LACKS "COUNTER SPACE." WHERE WOULD GRANDMA BABBAGE BE WITHOUT SOMEPLACE TO SET DOWN HER SPAGHETTI?



 
ALTHOUGH THE ALU CAN PERFORM MIRACLES OF INPUT/OUTPUT, IT CAN'T REMEMBER ANYTHING — AND THAT'S WHERE FLIP-FLOPS COME IN...



 
# FLIP-FLOPS

LATCH ON TO THIS!


VERSATILE AS THEY MAY BE, THE LOGICAL COMBINATIONS WE'VE BEEN SKETCHING STILL HAVE NO MEMORY. THEIR OUTPUT CONTINUES ONLY AS LONG AS THE INPUT IS APPLIED.



 **AND YET** — THERE IS A WAY TO HOOK THESE LOGICAL BUT SEMIWE GATES TOGETHER INTO A GADGET THAT HOLDS AN OUTPUT INDEFINITELY: THE FLIP-FLOP. STARE AT THIS A MINUTE !!





 


BESIDES THE STRANGE WAY A FLIP-FLOP EATS ITS OWN TAIL, PLEASE NOTE THE UNFAMILIAR GATE USED IN THE CONSTRUCTION. IT'S CALLED A

**NAND GATE**


WHICH IS MERELY AN ABBREVIATION OF "NOT-AND."

A	B	NAND
1	1	0
1	0	1
0	1	1
0	0	1

 


NOW FOR THE FLIP-FLOP IN ACTION:


SUPPOSE THE INPUT IS  $S=1, R=0$

 

 THEN  $\bar{Q}$  MUST BE 1, BECAUSE NAND OUTPUTS 1 IF EITHER INPUT IS 0. COUPLING THIS BACK TO THE UPPER GATE GIVES  $Q=0$ .




 AND IF  $S=0, R=1$ ? WELL, THAT'S JUST THE PREVIOUS DIAGRAM TURNED UPSIDE DOWN:




NOW WHAT HAPPENS WHEN THE INPUT **CHANGES?**

 
SUPPOSING WE BEGIN WITH THE INPUT ( $S=1, R=0$ ), WHAT DOES CHANGING IT TO ( $S=1, R=1$ ) DO TO THE FLIP-FLOP'S OUTPUT?



 
THE ANSWER IS: **NOTHING!** THE LOWER NAND-GATE'S INPUT BECOMES (0, 1), SO ITS OUTPUT  $\bar{Q}$  IS STILL 1, SO Q REMAINS 0.



 BUT PRECISELY THE SAME LINE OF REASONING SHOWS NO CHANGE IN OUTPUT WHEN INPUT CHANGES TO ( $S=1, R=1$ ) FROM ( $S=0, R=1$ ):



 
A LITTLE WEIRD, ISN'T IT? THE SAME INPUT ( $S=R=1$ ) CAN PRODUCE TWO DIFFERENT OUTPUTS, DEPENDING ON THE PREVIOUS INPUT!



THE WAY A FLIP-FLOP IS USED IS THIS: IT BEGINS BY SITTING THERE WITH A CONSTANT INPUT OF ( $S=1, R=1$ ) AND AN OUTPUT OF GOD-KNOWS-WHAT:



 YOU **SET** THE FLIP-FLOP [I.E., MAKE  $Q=1$ ] BY FLASHING A 0 MOMENTARILY DOWN THE S-WIRE, AND THEN RETURNING IT TO 1:




OR YOU CAN **RESET** IT [MAKE  $Q=0$ ] BY FLASHING A 0 DOWN THE R-WIRE, THEN RETURNING IT TO 1:



IN EITHER CASE, AS LONG AS ( $1,1$ ) KEEPS COMING IN, THE FLIP-FLOP WILL MAINTAIN ITS OUTPUT UNTIL IT'S CHANGED WITH ANOTHER INCOMING 0.



 THE ONLY INPUT COMBINATION WE HAVEN'T CHECKED IS ( $R=S=0$ ). IT'S EASY TO VERIFY THAT IT PRODUCES OUTPUT OF  $Q=\bar{Q}=1$ :




THE ANSWER IS NOT SO CLEAR: IT DEPENDS ON WHICH OUTPUT HAPPENS TO FLOP FIRST!! (ONE OF THEM MUST.)

IF  $\bar{Q}$  IS FIRST TO CHANGE, WE GET:




IF Q FLOPS FIRST, HOWEVER:

 

SINCE THERE IS **NO WAY** OF KNOWING WHICH OF THESE WILL ACTUALLY HAPPEN, AND WE DON'T WANT OUR FLIP-FLOPS IN RANDOM STATES, THE INPUT ( $S=0, R=0$ ) IS

 **DISALLOWED.**


WE CAN SUMMARIZE THE BASIC "RS" FLIP-FLOP LIKE SO:



S	R	Q	$\bar{Q}$
1	1	NO CHANGE	
1	0	0	1
0	1	1	0
0	0	DISALLOWED!	

FLIP-FLOP INPUTS ARE ALWAYS ARRANGED TO MAKE CERTAIN THE DISALLOWED STATE CANNOT ARRIVE.

GAAAH!

 

 
# A LITTLE EXERCISE:

HVALP!




A NOR-GATE IS A SHORTHAND WAY OF WRITING "NOT OR:"  
I.E.



I AM THE TRUTH!


A	B	NOR
1	1	0
1	0	0
0	1	0
0	0	1

 A BASIC RS FLIP-FLOP MAY ALSO BE MADE OUT OF NOR-GATES:




 1. WHAT IS THE OUTPUT WHEN  $R=0, S=1$ ? WHEN  $S=0, R=1$ ?
2. WHAT HAPPENS WHEN EACH OF THESE INPUT CONDITIONS CHANGES TO  $R=0, S=0$ ?
3. WHAT IS THE OUTPUT WHEN  $R=1, S=1$ ? WHAT HAPPENS WHEN THIS CHANGES TO  $R=0, S=0$ ?
4. WHAT INPUT COMBINATION MUST BE DISALLOWED?
5. IF  $R=0, S=0$ , HOW DO YOU SET THIS FLIP-FLOP (I.E., MAKE  $Q=1$ )? HOW DO YOU RESET IT?


BY THE WAY, A FLIP-FLOP IS ALSO CALLED A **LATCH**, BECAUSE IT "LOCKS IN" DATA.




# REGISTERS, COUNTERS, & GLITCHES

 

 IF THE FLIP-FLOP IS A DEVICE FOR STORING ONE BIT, A REGISTER STORES SEVERAL BITS SIMULTANEOUSLY. IT'S LIKE A ROW OF BOXES, EACH HOLDING ONE BIT.




A ROW OF FLIP-FLOPS SHOULD DO THE JOB...

 


...SORT OF! **BOOP** IF YOU TRY AND MAKE THIS WORK BY HOOKING UP SOME INPUTS TO RS FLIP-FLOPS, YOU MAY FIND YOURSELF GROWING CONFUSED!

 THE SOLUTION IS TO ADD A "GATING NETWORK" TO THE BASIC R-S FLIP-FLOP.




 HERE "D" STANDS FOR DATA, AND "E" STANDS FOR ENABLE. NOTE THAT THE GATING NETWORK MAKES IT IMPOSSIBLE FOR R AND S TO BE ZERO SIMULTANEOUSLY.




WHEN  $E=1$ , THEN  $R=D$  AND  $S=\bar{D}$  (NOT-D). HENCE, THE VALUE OF D IS STORED AT Q. IN OTHER WORDS,  $E=1$  **ENABLES**

 THE BIT D TO BE LOADED INTO THE FLIP-FLOP.




WHEN  $E=0$ , S AND R BOTH BECOME 1, AND THE FLIP-FLOP DOES NOT CHANGE. THAT IS,  $E=0$  BLOCKS THE ARRIVAL OF MORE DATA.

 
COMPUTERS ARE BLACK BOXES MADE OF BLACK BOXES MADE OF BLACK BOXES...



 SO - IN THE SPIRIT OF IGNORING THE INNER WORKINGS ONCE THEY'RE UNDERSTOOD [OR EVEN WITHOUT EVER UNDERSTANDING THEM], WE INCORPORATE THE GATING NETWORK INTO THE BOX, AND DRAW THE GATED LATCH LIKE SO




 THEN HERE'S A **PARALLEL REGISTER**: NOT THE ONLY KIND OF REGISTER, BUT A GENUINE MEMBER OF THE BREED!



ON  $E=1$ , FOUR BITS ARE SIMULTANEOUSLY LOADED INTO THE LATCHES!

NOW WHAT CONTROLS THE "ENABLE" INPUT?

 

A BASIC FACT OF COMPUTER LIFE:

AS SOON AS YOU BEGIN STORING DATA, QUESTIONS OF TIMING ARISE: HOW LONG DO YOU STORE IT? WHEN DO YOU MOVE IT? HOW DO YOU SYNCHRONIZE SIGNALS? THESE ISSUES ARE SO CRITICAL THAT LOGIC WITH MEMORY


IS CALLED SEQUENTIAL, TO DISTINGUISH IT FROM THE PURELY COMBINATIONAL LOGIC OF MEMORY-LESS NETWORKS. TO KEEP THE SEQUENTIAL LOGIC IN STEP,

# ALL COMPUTERS HAVE CLOCKS!


THE CLOCK'S PULSE IS THE COMPUTER'S HEARTBEAT—ONLY INSTEAD OF A WARM, RAGGED HUMAN HEARTBEAT, LIKE THIS—



THE COMPUTER'S PULSE IS SQUARE AND COLD:

 

 
ONE CLOCK PULSE IS THE BURST OF CURRENT WHEN CLOCK OUTPUT = 1. ONE CYCLE IS THE INTERVAL FROM THE BEGINNING OF A PULSE TO THE BEGINNING OF THE NEXT. DEPENDING ON THE COMPUTER, THE CLOCK FREQUENCY MAY BE HUNDREDS OF THOUSANDS TO BILLIONS OF CYCLES PER SECOND!




THE IDEA OF USING A CLOCK IS THAT THE COMPUTER'S LOGICAL STATE SHOULD CHANGE ONLY ON THE CLOCK PULSE. IDEALLY, WHEN THE CLOCK HITS 1, ALL SIGNALS MOVE, THEN STOP ON CLOCK = 0. THEN GO... THEN STOP... THEN GO...



 
A TYPICAL EXAMPLE IS TO ATTACH THE CLOCK TO THE "ENABLE" INPUT OF A GATED LATCH, IN WHICH CASE THE LATCH BECOMES KNOWN AS A "D FLIP-FLOP."



 UNFORTUNATELY, THINGS ARE RARELY IDEAL! IT TAKES A NON-ZERO TIME FOR A SIGNAL TO PASS ALONG A WIRE, SO THINGS ARE NEVER PERFECTLY SYNCHRONIZED. FOR EXAMPLE, SUPPOSE AT AN AND GATE, ONE INPUT IS CHANGING FROM 1 TO 0, AND THE OTHER FROM 0 TO 1.



 
IF A CHANGES AFTER B, THE OUTPUT WILL HAVE AN UNWANTED PULSE:



THAT PULSE IS A GLITCH, AND BRIEF AS IT IS, IT CAN CAUSE A FLIP-FLOP TO FLOP!




 THE GLITCH IS DEFEATED BY THE **MASTER-SLAVE** FLIP-FLOP:




WE WERE BORN EQUAL, MASTER AND ONLY MY POSITION MAKES ME A SLAVE!

 
THE INVERTED CLOCK SIGNAL TO THE SLAVE FLIP-FLOP DELAYS THE DATA INPUT FROM ARRIVING AT THE SLAVE UNTIL THE **END** OF A CLOCK PULSE, AFTER ALL GLITCHES HAVE DIED OUT. FOR EXAMPLE, SUPPOSE WE WANT TO LOAD THE BIT 1 INTO THE FLIP-FLOP.



 AS USUAL, WE DRAW THE WHOLE THING AS A SINGLE BOX!



 STRINGING A NUMBER OF MASTER-SLAVE FLIP-FLOPS TOGETHER MAKES A **SHIFT REGISTER**:



DATA ENTER A SHIFT REGISTER ONE BIT AT A TIME, SHIFTING TO THE RIGHT WITH EACH NEW CLOCK PULSE.

FOR EXAMPLE, THE NIBBLE 1101 WOULD ENTER THE SHIFT REGISTER LIKE THIS:



EACH CLOCK PULSE BRINGS A NEW BIT INTO THE REGISTER. (WHY DOESN'T THE BIT TRAVEL ALL THE WAY THROUGH ON ONE PULSE? BECAUSE OF THE MASTER-SLAVE FLIP-FLOPS!)

LIKewise, THE NIBBLE SHIFTS OUT ONE BIT AT A TIME.


SHIFT REGISTERS ARE USEFUL WHEN INFORMATION IS TO BE TRANSMITTED **SERIALLY**, OR ONE BIT AT A TIME.

FINALLY, A SPECIAL KIND OF REGISTER: THE **COUNTER**.

IS THAT LIKE THE COUNTER MONTE CRISTO?




 A COUNTER IS JUST WHAT IT SOUNDS LIKE: SOMETHING THAT COUNTS. IN OTHER WORDS, IT'S A REGISTER THAT **INCREMENTS** ITSELF—ADDS 1 TO ITS CONTENTS—WHENEVER A "COUNT" SIGNAL ARRIVES:




ETC!

 
DESCRIBED IN THAT WAY, A COUNTER SOUNDS EASY TO MAKE: JUST COMBINE AN ADDER WITH A REGISTER! THIS WOULD IN FACT WORK, BUT THERE'S AN EVEN SLICKER WAY, BASED ON ANOTHER FANCY FLIP-FLOP. CONSIDER THIS MASTER-SLAVE FLIP-FLOP, COUPLED BACK ON ITSELF:



ON  $E=1$ ,  $\bar{Q}$  GOES IN AT D:

 


 
ON  $E=0$ , D PASSES TO Q, AND THE OUTPUTS REVERSE.




E:



  THEN Q REVERSES ONCE FOR EACH CYCLE OF E—IN OTHER WORDS, Q **TOGGLES** JUST HALF AS OFTEN AS E:



 AS USUAL, WE ABBREVIATE THE WHOLE CIRCUIT BY THIS SIMPLER BOX. THE "T" IS FOR TOGGLE, TO INDICATE THAT THE FLIP-FLOP TOGGLES WHENEVER  $T=1$ . THEN HERE'S OUR COUNTER: EACH FLIP-FLOP TOGGING AT HALF THE RATE OF THE ONE TO ITS LEFT:




COUNT IN	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
...	...	...	...	...



A FEW ITEMS OF NOTE:


1

 THIS COUNTER IS CALLED AN "ASYNCHRONOUS RIPPLE COUNTER," BECAUSE THE COUNT RIPPLES THROUGH FROM ONE FLIP-FLOP TO THE NEXT. THIS CAUSES A SLIGHT DELAY BEFORE THE COUNT IS REGISTERED.



2

WHEN THE 16<sup>TH</sup> COUNT PULSE ARRIVES, THE COUNTER RETURNS TO 0. TO GO HIGHER THAN 15, MORE FLIP-FLOPS ARE NEEDED.

 

THIS 14-BIT COUNTER CAN GO FROM 0 TO  $2^{14}-1 = 16,383$


3

THE N<sup>TH</sup> FLIP-FLOP IN A RIPPLE COUNTER DIVIDES THE INCOMING PULSE BY  $2^N$ . THIS IS THE PRINCIPLE ON WHICH DIGITAL WATCHES ARE BASED: A HIGH-FREQUENCY INTERNAL CLOCK PULSE IS DIVIDED TO A RATE OF PRECISELY ONE CYCLE PER SECOND.



4

 THERE ARE ALSO SYNCHRONOUS COUNTERS, WHICH REGISTER ALL BITS SIMULTANEOUSLY, AND COUNTERS WHICH RETURN TO 0 ON ANY PREASSIGNED NUMBER. IN ANY CASE, FROM NOW ON, A COUNTER IS JUST ANOTHER BLACK BOX !!





EXERCISES

THE AMAZING NAND:



1. SHOW THAT

  


CONCLUDE THAT  $\Rightarrow$  ALL LOGIC CAN BE DERIVED FROM THE SINGLE RELATION NAND!!!

2. CAN THE SAME BE DONE WITH NOR?

3. SHOW THAT



IS THE SAME AS

 

REDRAW THE ADDER ON P. 126 USING ONLY NAND-GATES.

4. GIVEN A 4-BIT SHIFT REGISTER,



SHOW ITS CONTENTS AFTER EACH OF FOUR CLOCK PULSES AS THE NIBBLE 0011 IS ENTERED.

5. HOW WOULD YOU ATTACH A BUZZER TO A COUNTER TO SOUND WHEN THE COUNT HITS NINE (=1001 IN BINARY)? HINT: LOOK AT THE SEAT BELT BUZZER ON P. 109.

6. CONVINCE YOURSELF THAT ATTACHING INVERTERS TO THE OUTPUTS MAKES A COUNTER COUNT BACKWARDS.



NOW IN CASE YOU'RE FEELING STRANGLD BY SPAGHETTI—


THE TANGLED DIAGRAMS ON THE PRECEDING PAGES WERE NEVER INTENDED TO TRACE THE COMPLETE WIRING DIAGRAM OF ANY COMPUTER. RATHER, THEY ARE MEANT TO DEMONSTRATE HOW THE COMPUTER'S ESSENTIAL FUNCTIONS—MATH, COMPARISON, DECODING, DATA SELECTION AND STORAGE—ALL DEPEND ON SIMPLE LOGIC.



NOW THAT YOU PRESUMABLY BELIEVE IN THE POWER OF LOGIC, NO MORE WIRING DIAGRAMS ARE NEEDED!




ONWARD,  
TO HIGHER  
LEVELS!

 
 
# MEMORY



IN THE INFANCY OF ELECTRONIC COMPUTING, MEMORY WAS ALWAYS MORE EXPENSIVE THAN SHEER COMPUTING POWER. PLENTY OF PROCESSING COULD BE DONE WITH RELATIVELY FEW COMPONENTS, BUT EVERY INCREASE IN MEMORY SIMPLY MEANT **MORE** = MORE ACTUAL, PHYSICAL PLACES TO STORE THINGS!



SINCE THEN, RESEARCH INTO MEMORY TECHNOLOGY HAS BROUGHT DOWN THE COST CONSIDERABLY. FOR A FEW HUNDRED DOLLARS YOU CAN BUY A MICRO WITH OVER 64,000 BYTES OF MEMORY, COMPARED WITH ENIAC'S MEMORY OF ABOUT 100 NUMBERS\* — AT A COST OF MILLIONS!!

AND A HUMAN'S BILLIONS OF NEURONS, COSTING—?



\*ENIAC DID NOT COMPUTE IN BINARY.

THE SAME RESEARCH EFFORT, HOWEVER, HAS PRODUCED A BEWILDERING ARRAY OF MEMORY TYPES AND TECHNOLOGIES!!

CARD MEMORIES, TAPE MEMORIES, DRUM, DISK, BUBBLE, OPTICAL, CORE, CHARGE-COUPLED DEVICE, AND SEMICONDUCTOR MEMORIES; VOLATILE AND NON-VOLATILE, DYNAMIC AND STATIC, DESTRUCTIVE AND NON-DESTRUCTIVE, READ-WRITE, READ-ONLY, PROGRAMMABLE READ-ONLY, ERASABLE PROGRAMMABLE READ-ONLY...PANT:  
:PUFF:



WELL, ONE HAS TO BEGIN SOMEWHERE!!

AN IMPORTANT DISTINCTION EXISTS BETWEEN

# ELECTRONIC


AND

# ELECTRO-MECHANICAL

MEMORY DEVICES.

ELECTRONIC MEMORIES, WITH NO MOVING PARTS, ARE AS FAST AS THE REST OF THE COMPUTER.

 
ELECTROMECHANICAL MEMORIES HAVE MOVING PARTS, LIKE DISKS OR REELS OF TAPE. THIS MAKES THEM SLOW—HOW SLOW DEPENDING ON THE TYPE OF MEMORY.




ELECTRONIC MEMORIES' SPEED MAKES THEM IDEAL FOR THE COMPUTER'S MAIN, OR INTERNAL MEMORY, WHILE ELECTRO-MECHANICAL MEMORIES ARE USED FOR AUXILIARY STORAGE OUTSIDE THE MACHINE.

ELECTROMAGNETIC MEMORIES COMPENSATE FOR THEIR SLOWNESS WITH A GIGANTIC CAPACITY. ONE HARD DISK CAN STORE UP TO TEN MILLION BYTES, COMPARED WITH A TYPICAL MICRO'S MAIN MEMORY OF 65,536 ( $=2^{16}$ ) BYTES.

 
INTERNAL MEMORY CAN BE THOUGHT OF AS A SIMPLE GRID, WITH A CELL AT EACH INTERSECTION. DEPENDING ON THE COMPUTER, EACH CELL CAN HOLD ONE BYTE, TWO BYTES, OR MORE.



 EVERY CELL HAS A UNIQUE ADDRESS, SPECIFYING WHERE IT SITS IN THE GRID.



 
IN PRACTICE, THERE MAY BE MANY SUCH GRIDS, IN WHICH CASE THE ADDRESS SPECIFIES THE GRID NUMBER, AS WELL AS THE ROW AND COLUMN WITHIN IT.



 **NOTE:**

DO NOT CONFUSE A CELL'S ADDRESS WITH ITS CONTENTS !!

WHAT IS THE MAXIMUM NUMBER OF CELLS THE COMPUTER CAN ADDRESS? THIS DEPENDS ON THE LENGTH AND STRUCTURE OF THE COMPUTER'S "WORDS." FOR EXAMPLE, A 32-BIT MACHINE MAY INTERPRET THE FIRST 8 BITS AS AN INSTRUCTION...



... AND THE REMAINING 24 BITS AS AN ADDRESS.

IN THAT CASE, ADDRESSES CAN BE ANYTHING BETWEEN


00000...0  
AND

1111...1 =  $2^{24} - 1$

GIVING  $2^{24}$  POSSIBLE MEMORY CELLS.



 AN 8-BIT MICRO, ON THE OTHER HAND, MIGHT PROCESS THREE BYTES IN SUCCESSION:



AN INSTRUCTION,




THE FIRST HALF OF AN ADDRESS,




AND THE SECOND HALF OF AN ADDRESS.

 ▶ HERE THE ADDRESS IS 16 BITS LONG, GIVING  $2^{16} = 65,536$  POSSIBLE ADDRESSES.



 16-BIT WORDS ARE OFTEN SPLIT LIKE THIS INTO HIGHER-LEVEL AND LOWER-LEVEL BYTES.



TO MAKE ADDRESSES SHORTER AND MORE READABLE, THEY'RE OFTEN EXPRESSED IN

**HEXADECIMAL,**

OR BASE-16, NUMERALS.

10<sub>HEX</sub> = 16<sub>DECIMAL</sub>

100<sub>HEX</sub> =  $16^2 = 256$

1000<sub>HEX</sub> =  $16^3 = 4096$

⋮  
ETC!



JUST AS BASE-10 NUMBERS REQUIRE THE DIGITS 0-9, SO HEXADECIMAL NEEDS DIGITS FROM 0 TO FIFTEEN. THE EXTRAS ARE REPRESENTED BY THE LETTERS A-F:

DECIMAL	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
HEX	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F

FOR EXAMPLE:

4A0D<sub>HEX</sub> =

$4 \times 16^3$


$+ 10 \times 16^2$

$+ 0 \times 16$

$+ 13 \times 1$

18,957<sub>DECIMAL</sub>

 TO CONVERT BINARY TO HEX: GROUP THE BINARY NUMBER INTO NIBBLES, STARTING FROM THE RIGHT. CONVERT EACH NIBBLE TO A HEX DIGIT!




TO CONVERT HEX TO BINARY, JUST REVERSE THE PROCESS.

FROM THE HARDWARE POINT OF VIEW, THERE ARE THREE MAIN TYPES OF INTERNAL MEMORY.
 
# CORE

MEMORIES USE LITTLE MAGNETIC DOUGHNUTS - "CORES." EACH CORE CAN BE ELECTRICALLY MAGNETIZED IN ONE OF TWO DIRECTIONS, REPRESENTING 0 AND 1.



AND TWO SEMICONDUCTOR MEMORIES:


# RAM

USES FLIP-FLOPS TO STORE BITS - SO EACH MEMORY CELL IS ESSENTIALLY A (PARALLEL) REGISTER!


 
# ROM

INDICATES A 1 OR 0 AT EACH GRID POINT BY THE PRESENCE OR ABSENCE OF AN ELECTRIC CONNECTION THERE.



# RAM

STANDS FOR "RANDOM ACCESS MEMORY," MEANING THAT ANY CELL CAN BE ACCESSED DIRECTLY. ROM AND CORE MEMORIES ALSO PROVIDE RANDOM ACCESS, BUT FOR SOME REASON RAM HOGGED THE NAME!




A CASE OF SPECIES CONFUSSION...


# ROM

STANDS FOR "READ-ONLY MEMORY."

ROM-AN STYLE LETTERING

 


RAM

 

ROM


THE PRACTICAL DIFFERENCE BETWEEN THEM IS THAT YOU CAN ONLY READ WHAT'S IN ROM, WHILE WITH RAM YOU CAN READ THINGS OUT OR WRITE THEM IN WITH EQUAL EASE.

IN GENERAL!

 

WHEN YOU LOAD A PROGRAM INTO THE COMPUTER, IT IS STORED IN RAM.


UNFORTUNATELY,  
RAM IS  
**VOLATILE,**

 


**MEANING** → IT FORGETS EVERYTHING WHEN THE POWER IS TURNED OFF.

FOR EXAMPLE, I OWN A BATTERY-POWERED POCKET COMPUTER WITH 1680 BYTES OF RAM. IT CAN STORE UP TO TEN PROGRAMS EVEN WHEN I TURN IT OFF, BECAUSE IT KEEPS SOME ELECTRICITY RUNNING THROUGH MEMORY.

 BUT WHEN THE BATTERY DIES... BYE BYE, PROGRAMS!




 RAM VOLATILITY IS ONE REASON THAT THE MAGNIFICENT, INFALLIBLE COMPUTER IS VULNERABLE TO THE VAGARIES OF OUTMODDED, ERRATIC POWER GENERATING STATIONS!




**ROM** - "READ-ONLY MEMORY" -  
ONCE ITS CONTENTS ARE ENTERED, CAN NEVER BE REWRITTEN.\*  
ORDINARILY, ROM IS PROGRAMMED AT THE FACTORY, BUT THERE ARE NOW ALSO **PROMS** - PROGRAMMABLE ROMS - WHICH CAN BE CUSTOM-PROGRAMMED TO THE USER'S SPECIFICATIONS.

 \*EXCEPT FOR EPROM - ERASABLE PROGRAMMABLE ROM - BUT WE WON'T GET INTO THAT!



 UNLIKE RAM, ROM IS **NON-VOLATILE**:  
IT KEEPS ITS CONTENTS EVEN WITHOUT POWER. AFTER ALL, IT'S NOTHING BUT A HUGE GRID OF WIRES WITH PHYSICAL CONNECTIONS AT SOME INTERSECTIONS. THE CONNECTIONS REMAIN, REGARDLESS OF ELECTRIC CURRENT.






 
## SOME TYPICAL USES OF ROM:

MOST VIDEO GAME CARTRIDGES ARE PROGRAMMED IN ROM. JUST PLUG IT IN AND IT'S READY TO GO! BUT OF COURSE, IT CAN'T BE REPROGRAMMED EITHER...

YOU WANT TO PLAY ANOTHER GAME, YOU BUY ANOTHER GAME, SON..




 MANY PERSONAL COMPUTERS HAVE THOUSANDS OF BYTES OF ROM TO STORE THE PROGRAM WHICH IN TURN ALLOWS THE MACHINE TO "UNDERSTAND" THE LANGUAGE CALLED BASIC.



AND, AS WE'LL SEE, ROM PLAYS AN IMPORTANT ROLE IN THE COMPUTER'S CONTROL SECTION.

 BEHIND THE EXPLOSIVE GROWTH OF RAM AND ROM IS... THE INCREDIBLE SHRINKING TECHNOLOGY!



ETCHED ON SILICON CHIPS, THE DENSITY OF COMPONENTS PER CHIP HAS BEEN DOUBLING EVERY YEAR!




THE STANDARD MEASURE OF CHIP STORAGE IS THE **K**, SHORT FOR "KILO" ("CHIL" IS GREEK FOR 1000), IN COMPUTERESE IT MEANS  $2^{10}$ , THE POWER OF TWO CLOSEST TO 1000:

ALMOST GREEK FOR ALMOST 1000!


 
# K = 1024

THE FIRST RAM CHIP WITH 1K BITS OF STORAGE WAS A SENSATION — BUT NOW 64 K IS COMMON, AND THE 256K CHIP HAS ARRIVED! WHAT'S NEXT?







DESPITE THE GROWTH OF RAM CAPACITY,  
SOMETIMES IT IS NOT THE ANSWER TO  
EVERY PRAYER !!

SHOW US  
THE WAY TO  
STORE  
**MORE**  
THAN INTERNAL  
RAM CAN  
HOLD!

LET US  
PROTECT  
OUR DATA  
FROM  
POWER  
LOSSES!

GRANT  
US A PROGRAM  
LIBRARY OF  
FREQUENTLY  
USED  
ROUTINES!

GIVE  
US  
LASER-  
POWERED  
GADGETS!

  

THE ANSWER?

## mass storage.

AS THE NAME IMPLIES,  
MASS STORAGE IS MEMORY  
THAT CAN STORE A LOT!!  
ALMOST ALL MASS STORAGE  
DEVICES ARE NON-VOLATILE  
AND HAVE A MECHANICAL  
COMPONENT THAT MAKES THEM  
MUCH SLOWER THAN ELECTRONIC  
RANDOM ACCESS MEMORIES.




FOR EXAMPLE:


 
## PUNCH CARDS.

THE CARDS OF JACQUARD, BABBAGE,  
AND HOLLERITH ARE STILL IN USE!



## PAPER TAPE

SAME IDEA AS PUNCH CARDS: A HOLE REPRESENTS  
1, A NON-HOLE 0.



## MAGNETIC TAPE


STORES BITS AS SMALL MAGNETIC REGIONS, WHICH MAY  
BE MAGNETIZED IN ONE OF TWO DIRECTIONS,  
REPRESENTING 1 OR 0.




FASTER, LESS BULKY, AND THE CURRENT STORAGE OF CHOICE IS THE



 
DISKS ALSO STORE BITS AS TINY MAGNETIZED REGIONS — UP TO 10 MILLION BYTES PER DISK!



 A BIG COMPUTER SYSTEM USUALLY HAS MULTIPLE DISK DRIVES, WITH PHONOGRAPH-ARMLIKE READ/WRITE HEADS DARTING BACK AND FORTH ACROSS THE WHIRLING PLATTERS.




 ARE SMALL, LOW-COST MAGNETIC DISKS MADE OF PLASTIC. THEY ALWAYS STAY IN THEIR JACKETS, BECAUSE A SPECK OF DUST CAN CREATE A MONSTER GLITCH!



OTHER, MORE EXOTIC MASS STORAGE TECHNOLOGIES INCLUDE BUBBLE MEMORIES, CHARGE-COUPLED DEVICES, AND OPTICAL DISKS READ BY LASERS.


 
LIKE INTERNAL MEMORY, MASS STORAGE MUST BE ORGANIZED, OR "FORMATTED." TAKE THE FLOPPY DISK FOR EXAMPLE:



FLOPPIES ARE FORMATTED INTO RINGS AND SECTORS — THREE RINGS AND EIGHT SECTORS, IN THIS VERY OVER-SIMPLIFIED DISK. (IT'S MORE LIKE 26 SECTORS AND 77 RINGS IN A GENUINE DISK.)

TO ACCESS A PARTICULAR BLOCK OF DATA, YOU SPECIFY THE RING NUMBER AND SECTOR NUMBER. THEN THE DISK DRIVE

  
- 1) SPINS THE DISK UNTIL THAT SECTOR LIES UNDER THE READ/WRITE HEAD
- 2) MOVES THE HEAD IN OR OUT TO THE PROPER RING.



THIS PROCESS TAKES MILLISECONDS — AN ETERNITY TO A COMPUTER!
 
# SOME TYPICAL USES OF MASS STORAGE:

A GERBIL RANCHER,  
USING A MICROCOMPUTER  
TO IMPROVE PRODUCTIVITY,  
BUYS THE APPROPRIATE  
PROGRAMS (FROM GERBYTE,  
INC.) STORED ON  
FLOPPIES.



THE ONLY  
PEOPLE  
WHO CAN  
SEE THIS  
LIST ARE  
PEOPLE  
WHO AREN'T  
ON THIS  
LIST..



AND EVERYBODY'S  
ON THIS LIST...

A GOVERNMENT  
AGENCY (TAKE  
YOUR PICK)  
MAINTAINS FILES  
ON THE CITIZENRY, STORED  
ON HARD DISK...

SO WHO AM I?

THE PHONE COMPANY  
STORES IN BUBBLE  
MEMORY THE MESSAGE:  
"THE NUMBER YOU HAVE  
REACHED IS NOT IN  
SERVICE..."




HM... SOUNDS  
LIKE A  
VERBAL  
GERBIL...


WELL, YOU GET THE PICTURE...  
NOW IT'S TIME TO MOVE ON...
 
# GETTING EVERYTHING UNDER CONTROL


IN WHICH ALL  
THE BLACK BOXES  
ARE FINALLY SEEN  
TO FIT TOGETHER...



 ALONG WITH INPUT/OUTPUT, MEMORY AND THE ARITHMETIC-LOGIC UNIT, CONTROL IS THE COMPUTER'S FINAL, CRITICAL INGREDIENT. OUR OLD SCHEMATIC DIAGRAM SHOWS THE FLOW OF CONTROL (→) AND INFORMATION (⇌).



 IT HELPS TO REDRAW THIS DIAGRAM IN A WAY THAT BETTER REFLECTS A GENUINE COMPUTER DESIGN KNOWN AS "BUS ARCHITECTURE."




THE VERTICAL ARROWS, REPRESENTING ELECTRICAL PATHWAYS A BYTE OR MORE WIDE, ARE THE BUSES.

ACCORDING TO SIGNALS PASSED ALONG THE CONTROL BUS, ADDRESSES AND DATA GET ON AND OFF THE DATA/ADDRESS BUS, WITH THE PROVISION THAT ONLY ONE "PASSENGER" CAN RIDE THE BUS AT A TIME.

NOTE THAT ALL THE ARROWS ON THE CONTROL BUS POINT AWAY FROM THE CONTROL SECTION.

HOW ARE WE TO IMAGINE THIS CONTROL, FROM WHICH ALL DARK ARROWS POINT AWAY??

 
AS A MEGALOMANIACAL ROBOT THAT CAN'T KEEP ITS ELECTRONIC FINGERS OUT OF ANYTHING?




A WISE RULER WHO JUDICIOUSLY CHOOSES THE TIME FOR EVERY ACT?



 A RELENTLESS TYRANT WHO WIELDS A WHIP OVER REBELLIOUS GLITCHES?



 LIKE ANYONE ELSE, CONTROL REVEALS ITS CHARACTER BY ITS BEHAVIOR... SO LET'S FOLLOW WHAT HAPPENS IN THIS OVERSIMPLIFIED COMPUTER, WHICH FLESHES OUT THE DIAGRAM OF TWO PAGES BACK WITH SOME ESSENTIAL COUNTERS AND REGISTERS.



THIS IS A MINIMAL COLLECTION OF EQUIPMENT. A TYPICAL COMPUTER HAS MORE REGISTERS AND COUNTERS, BUT ALL COMPUTERS HAVE THE ONES SHOWN HERE.

HERE'S WHAT THEY'RE FOR:

PROGRAM COUNTER:  
TICKS OFF THE INSTRUCTIONS ONE BY ONE.

Two...  
Two...?



INSTRUCTION REGISTER:  
HOLDS AN ENCODED VERSION OF THE INSTRUCTION BEING PERFORMED.

"BOIL SPAGHETTI TEN MINUTES."



ADDRESS REGISTER:  
HOLDS THE ADDRESS OF WHATEVER IS TO ENTER OR LEAVE MEMORY.

GET ME  
BYTE  
#0101!



ACCUMULATOR:  
THE ALU'S MAIN REGISTER, KEEPING A RUNNING TOTAL OF ALU OPERATIONS.

COULDN'T SOLVE 1+1 WITHOUT IT!



B REGISTER:  
AN AUXILIARY REGISTER TO HOLD NUMBERS ON THEIR WAY TO ALU.

LIKE A MOTEL THAT RENTS ROOMS BY THE MICROSECOND!




C REGISTER:  
HOLDS DATA ON THE WAY TO OUTPUT.

IS THERE CONTROL IN THE OUTSIDE WORLD?



IN FACT, CONTROL SPENDS MOST OF ITS TIME JUST MOVING THE CONTENTS OF THESE REGISTERS AROUND!

 TO SEE HOW CONTROL WORKS, LET'S FOLLOW WHAT HAPPENS WHEN THE COMPUTER **ADDS TWO NUMBERS** - OUR VERY FIRST PROGRAM!




LIKE EVERYTHING ABOUT COMPUTERS, PROGRAMS CAN BE DESCRIBED AT VARIOUS LEVELS. WE BEGIN WITH

## ASSEMBLY LANGUAGE,

WHICH SPECIFIES THE COMPUTER'S ACTUAL MOVES, BUT OMITTS THE FINE DETAILS. AT THIS LEVEL, HERE'S HOW TO ADD TWO NUMBERS:

 0. LOAD THE FIRST NUMBER INTO THE ACCUMULATOR.
1. ADD THE SECOND NUMBER (HOLDING THE SUM IN THE ACCUMULATOR).
2. OUTPUT THE CONTENTS OF THE ACCUMULATOR.
3. HALT.



TO EXPRESS THIS IN PROPER ASSEMBLY LANGUAGE, WE MUST SPECIFY THE PRECISE LOCATION IN MEMORY OF THE TWO NUMBERS TO BE ADDED, AND CONDENSE THE WORDY STATEMENTS INTO MNEMONIC\* ABBREVIATIONS. SUPPOSE, FOR EXAMPLE, THAT THE NUMBERS ARE STORED AT ADDRESSES 1E AND 1F (HEXADECIMAL). OUR PROGRAM BECOMES:



- |           |  |
|-----------|--|
| 0. LDA 1E | ("LOAD ACCUMULATOR WITH CONTENTS OF 1E") |
| 1. ADD 1F | ("ADD CONTENTS OF 1F")                   |
| 2. OUT    | ("OUTPUT CONTENTS OF ACCUMULATOR.")      |
| 3. HALT   |  |

\*MNEMONIC = MEMORY-AIDING



IN GENERAL, ASSEMBLY-LANGUAGE STATEMENTS HAVE TWO PARTS:


THE **OPERATOR**, WHICH DESCRIBES THE STEP TO BE PERFORMED

THE **OPERAND**, WHICH GIVES THE ADDRESS ON WHICH THE OPERATOR ACTS



NOTE HOWEVER! SOME OPERATORS DON'T NEED AN EXPLICIT OPERAND. "OUT" FOR INSTANCE IS UNDERSTOOD TO APPLY TO THE ACCUMULATOR.


FEED ME!

 

NOW THAT WE HAVE AN ASSEMBLY-LANGUAGE PROGRAM, HOW DO WE FEED IT TO THE MACHINE — WHICH ONLY UNDERSTANDS 0'S AND 1'S?



 THE ANSWER IS CLEAR: WITHIN THE MACHINE, EACH OPERATOR IS ENCODED AS A STRING OF BITS CALLED ITS "OP-CODE." SOME SIMPLE SAMPLES:




TO ME, "001" MEANS "LDA!"

OPERATOR	OP-CODE
LDA	001
ADD	010
OUT	110
HALT	111

I STILL WANT TO KNOW WHAT "MEAN" MEANS!



 THEN A MACHINE INSTRUCTION CONSISTS OF AN OP-CODE SEGMENT, OR "FIELD," FOLLOWED BY AN ADDRESS FIELD GIVING THE OPERAND IN BINARY:



SO HERE'S OUR PROGRAM TRANSLATED INTO MACHINE LANGUAGE:

0. LDA 1E	001 11110
1. ADD 1F	010 11111
2. OUT	110 XXXXX
3. HALT	111 XXXXX

ANY 5 BITS ARE O.K. FOR THESE ADDRESS FIELDS, AS THEY'LL BE IGNORED!

NOW

(ASSUMING AN INPUT DEVICE)

THE PROGRAM STEPS ARE READ INTO CONSECUTIVE MEMORY ADDRESSES, BEGINNING WITH 0. THE CONTENTS OF MEMORY ARE THEN

ADDRESS	CONTENTS
0	001 11110
1	010 11111
2	110 00000
3	111 00000

NOTE THAT THE PROGRAM STEP NUMBER IS THE ADDRESS WHERE IT'S STORED!




AND WE ALSO NEED TO ENTER THE DATA: THE TWO NUMBERS TO BE ADDED. ANY TWO NUMBERS WILL DO, SAY 5 AND 121. THEY GO IN ADDRESSES 1E AND 1F:

1E	00000101
1F	01111001



 
HOW CAN THE COMPUTER DISTINGUISH DATA FROM INSTRUCTIONS? BY ASSUMING EVERYTHING IS AN INSTRUCTION, UNLESS INSTRUCTED TO DO OTHERWISE!




ONCE THE PROGRAM IS STORED, CONTROL CAN BEGIN EXECUTION, IN A SERIES OF EVEN MORE PRIMITIVE STEPS CALLED MICROINSTRUCTIONS, ONE MICROINSTRUCTION OCCURRING WITH EACH CLOCK PULSE. ARE YOU READY FOR THE GORY DETAILS?

CONTROL BEGINS BY **FETCHING** THE FIRST INSTRUCTION. IT—

 0.0. MOVES CONTENTS OF PROGRAM COUNTER (00000000 TO BEGIN WITH) TO ADDRESS REGISTER




 0.1 MOVES CONTENTS OF THAT MEMORY ADDRESS TO INSTRUCTION REGISTER




THE INSTRUCTION REGISTER NOW HOLDS THE FIRST INSTRUCTION. CONTROL "READS" IT AND—

 0.2. MOVES THE INSTRUCTION REGISTER'S ADDRESS FIELD TO ADDRESS REGISTER



 0.3. MOVES CONTENTS OF THAT MEMORY ADDRESS TO ACCUMULATOR



THE ACCUMULATOR IS NOW LOADED WITH THE FIRST PIECE OF DATA. ONE MICROINSTRUCTION REMAINS:


0.4 INCREMENT PROGRAM COUNTER




A BIT CONFUSED? LET'S GO THROUGH IT AGAIN WITH THE NEXT STEP, **ADD**.

AGAIN CONTROL BEGINS WITH A "FETCH PHASE":

 1.0 MOVE CONTENTS OF PROGRAM COUNTER (NOW 00000001) TO ADDRESS REGISTER




 1.1 MOVE CONTENTS OF THAT ADDRESS TO INSTRUCTION REGISTER



THE INSTRUCTION IN THE INSTRUCTION REGISTER, 01011111, CAUSES CONTROL TO:

 1.2 MOVE ADDRESS FIELD FROM INSTRUCTION REGISTER TO ADDRESS REGISTER



1.3 MOVE CONTENTS OF THAT MEMORY ADDRESS TO B REGISTER



1.4 SIGNAL THE ALU TO **ADD** AND PUT THE SUM IN ACCUMULATOR



AGAIN, THERE'S ONE MORE STEP:

1.5 INCREMENT PROGRAM COUNTER






# AND FINALLY?


WELL, LUCKILY THE LAST TWO INSTRUCTIONS ARE EASIER:

 2.0 AND 2.1 ARE THE SAME FETCH INSTRUCTIONS AS BEFORE, PUTTING INSTRUCTION 2 ("OUT") IN THE INSTRUCTION REGISTER:



THIS OP-CODE (110) CAUSES CONTROL TO -

 2.2. MOVE CONTENTS OF ACCUMULATOR TO C REGISTER




2.3. INCREMENT PROGRAM COUNTER


FINALLY CONTROL FETCHES THE INSTRUCTION 111 ("HALT"), WHICH CAUSES CONTROL TO -

 3.2 DO NOTHING

ARE YOU BEGINNING TO SEE WHAT KIND OF BEAST CONTROL REALLY IS??



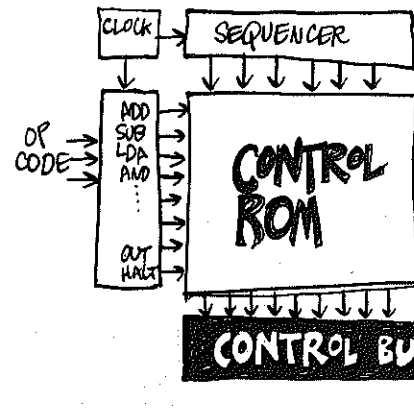
WITHOUT TOO MANY DETAILS, YOU CAN THINK OF CONTROL ROUGHLY LIKE THIS:



ITS INPUT CONSISTS OF CLOCK PULSES AND OP-CODES. ITS OUTPUT CONSISTS OF A SEQUENCE OF SIGNALS TO THE REGISTERS, COUNTERS, ALU, AND MEMORY.

THE "MICROPROGRAM," WHICH CONNECTS THE INPUTS TO THE PROPER OUTPUT COMBINATIONS, IS STORED IN A READ-ONLY MEMORY DEDICATED STRICTLY TO THIS PURPOSE.

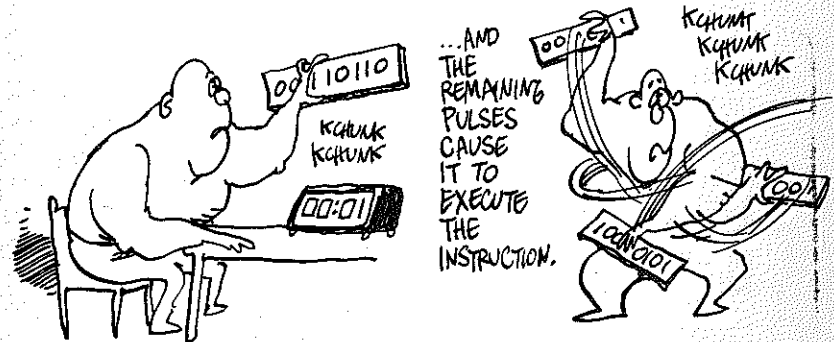THE FIRST COUPLE OF CLOCK PULSES CAUSE CONTROL TO FETCH AN INSTRUCTION...



...AND THE REMAINING PULSES CAUSE IT TO EXECUTE THE INSTRUCTION.



IN REAL LIFE THE SITUATION IS MORE COMPLICATED IN DETAIL BUT THE SAME IN PRINCIPLE. THERE ARE MORE REGISTERS, AND OP-CODES ARE LONGER THAN THREE BITS, ALLOWING CONTROL TO RESPOND TO A MUCH LARGER SET OF INSTRUCTIONS. HERE'S THE INSTRUCTION SET OF A GENUINE PROCESSOR, THE MOTOROLA 6800.

### ARITHMETIC

ADD  
ADD WITH CARRY  
SUBTRACT  
SUBTRACT WITH CARRY  
INCREMENT  
DECREMENT  
COMPARE  
NEGATE

### LOGICAL

AND  
OR  
EXCLUSIVE OR  
NOT  
SHIFT RIGHT  
SHIFT LEFT  
SHIFT RIGHT ARITHMETIC  
ROTATE RIGHT  
ROTATE LEFT  
TEST

### DATA TRANSFER

LOAD  
STORE  
MOVE  
CLEAR  
CLEAR CARRY  
CLEAR OVERFLOW  
SET CARRY  
SET OVERFLOW

### BRANCH

BRANCH  
BRANCH IF ZERO  
BRANCH IF NOT ZERO  
BRANCH IF EQUAL  
BRANCH IF NOT EQUAL  
BRANCH IF CARRY  
BRANCH IF NO CARRY  
BRANCH IF POSITIVE  
BRANCH IF NEGATIVE  
BRANCH IF OVERFLOW  
BRANCH IF NO OVERFLOW  
BRANCH IF GREATER THAN  
BRANCH IF GREATER THAN OR EQUAL  
BRANCH IF LESS THAN  
BRANCH IF LESS THAN OR EQUAL  
BRANCH IF HIGHER  
BRANCH IF NOT HIGHER  
BRANCH IF LOWER  
BRANCH IF NOT LOWER

### SUBROUTINE CALL

CALL SUBROUTINE

### SUBROUTINE RETURN

RETURN FROM SUBROUTINE  
RETURN FROM INTERRUPT

### MISCELLANEOUS

NO OPERATION  
PUSH  
POP  
WAIT  
ADJUST DECIMAL  
ENABLE INTERRUPT  
DISABLE INTERRUPT  
BREAK

ONE GROUP OF THESE INSTRUCTIONS DESERVES SPECIAL MENTION: THE **BRANCH, OR JUMP, INSTRUCTIONS.**

AS WE'LL SEE, THESE GIVE THE COMPUTER A LOT OF ITS "INTELLIGENCE." THEIR EFFECT IS TO **TRANSFER CONTROL** TO ANOTHER PART OF THE PROGRAM. THE SIMPLEST JUMP INSTRUCTION IS JUST PLAIN "JUMP," AS IN:

**JMP 123**




⇒ "JMP 123" CAUSES CONTROL TO ENTER 123 IN THE PROGRAM COUNTER... AND PROCEED WITH THE PROGRAM FROM THERE.


EVEN "SMARTER" ARE CONDITIONAL JUMPS. THEY TRANSFER CONTROL IF SOME CONDITION IS SATISFIED: FOR INSTANCE, "JUMP IF ZERO" MEANS JUMP IF THE ACCUMULATOR HOLDS 0.

**JZ 321**

OTHERWISE DON'T JUMP!

 

 SO YOU SEE,  
CONTROL IS  
NO TYRANT  
AT ALL. IT  
ONLY DOES  
WHAT IT'S TOLD—  
COMPLETELY  
AUTOMATICALLY!!



IF YOU REALLY WANT TO IMAGINE THE CONTROL SECTION'S  
PERSONALITY, THINK OF A PERFECTLY EFFICIENT  
BUREAUCRAT, ACTING IN STRICT OBEDIENCE TO THE  
COMPUTER'S REAL BOSS: THE **PROGRAM!**



PART III

SOFTWARE

